

SI100B


Introduction to Information Science and Technology (Electrical Engineering)

Lecture #3 (Digital) Combinational Logic Circuits

Instructor: Junrui Liang (梁俊睿)

Sept. 23rd, 2022

The Theme Story

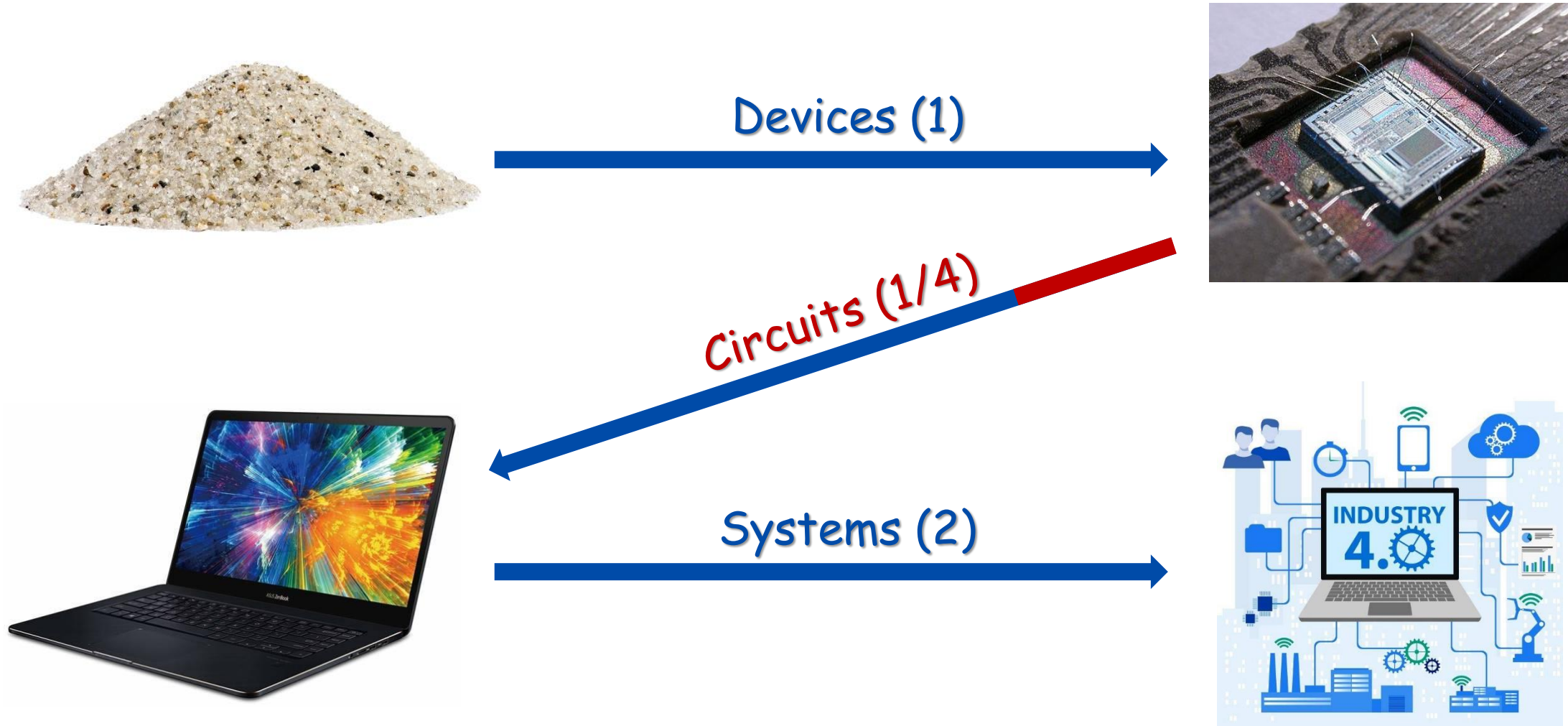

(Pictures are from the Internet)


Study Purpose of Lecture #3

- 哲学 (bao'an) 三问
 - Who are you?
 - Where are you from?
 - Where are you going?

To answer those questions
throughout your life



 - In this lecture, we ask
 - How many categories of circuits are there?
 - Why digital circuits 数字电路 won in computation & communication?
 - How to build combinational logic circuits 组合逻辑电路?



Lecture Outline


1. Circuit categories 电路种类
2. Boolean logic 布尔逻辑
3. Logic gates 逻辑门电路
4. Combinational logic circuit 组合逻辑电路
 - Example: majority circuit 投票选举电路实例

----- (break) -----


5. Combinational Logic Circuits Design 组合逻辑电路设计
 - Boolean algebra 布尔代数
 - Truth table 真值表
 - Karnaugh map 卡诺图
 - Example: decoder design 解码器设计实例

Four typical circuit categories


- Passive 被动/无源

 


- Digital 数字

 


- Analog 模拟

 

- RF 射频

 


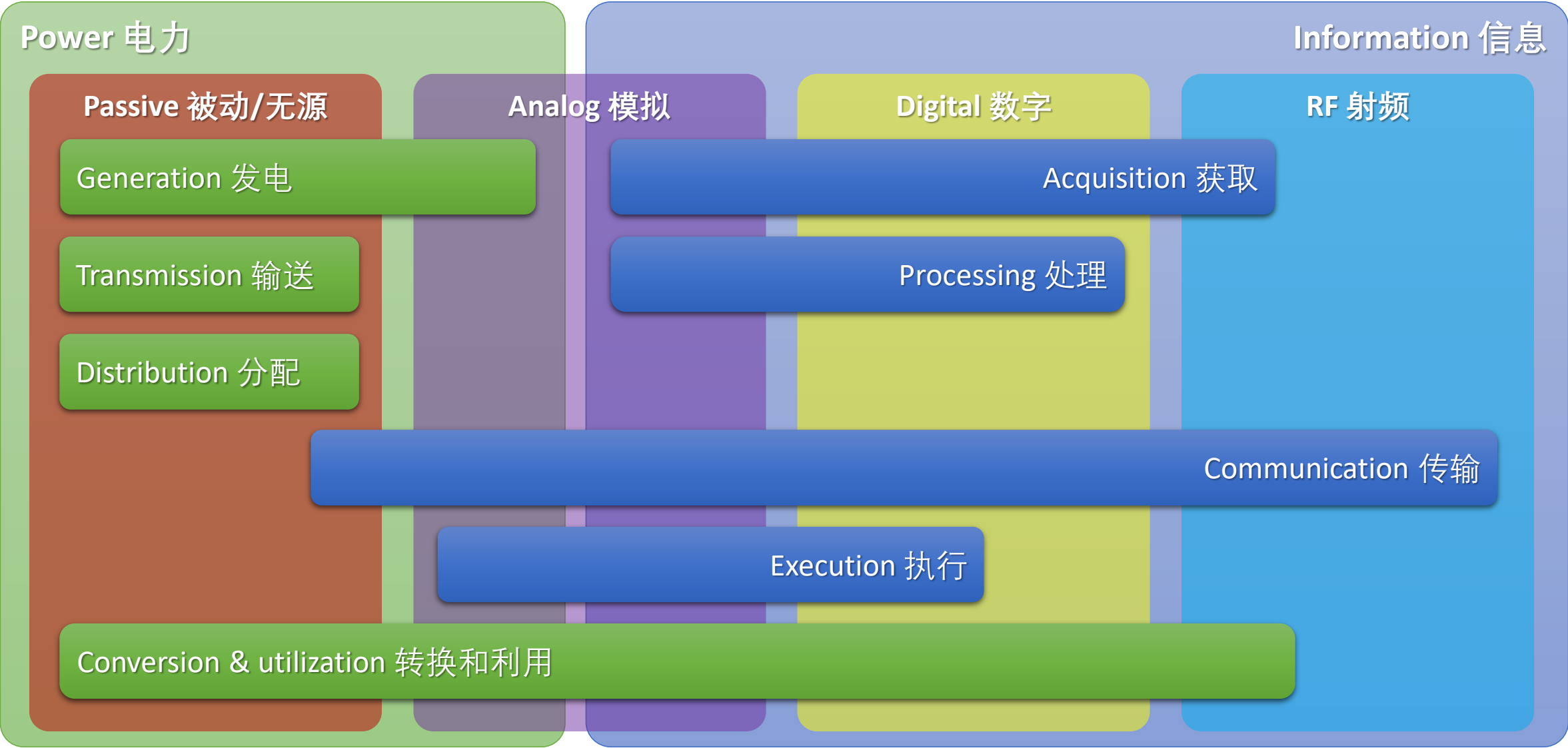Electrical circuits for different application purposes



Boolean logic

- George Boole
(1815 - 1864)

 


- Values


- Boolean algebra allows only two values—0 and 1
- The beauty of the *digital abstraction* is that digital designers can focus on 1's and 0's, ignoring whether the Boolean variables are physically represented with specific voltages, rotating gears, etc.

- Basic operations

 - AND (conjunction) 与 xy
- OR (disjunction) 或 $x + y$
- NOT (negation) 非 \bar{x}



$x \wedge y$

 

$x \vee y$



$\neg x$


Logic 0	Logic 1
False	True
Off	On
LOW	HIGH
No	Yes
Open switch	Closed switch

x	y	$x \wedge y$	$x \vee y$	x	$\neg x$
0	0	0	0	0	1
1	0	0	1	1	0
0	1	0	1		
1	1	1	1		

Basic logic gates

- NOT gate
- OR gate
- AND gate


NOT

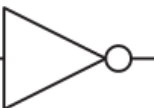

$Y = \bar{A}$

A	Y
0	1
1	0


OR



$Y = A + B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


AND

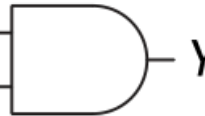

$Y = AB$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

AND4




$Y = ABCD$

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

- Buffer



BUF

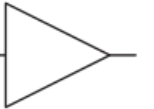


$Y = A$

A	Y
0	0
1	1


Logic gate implementation

  


• Mechanical way

 

• Electrical way

 

Schematic

 


Physical layout

A 3D-view of the CMOS implementation


INVERTER




Input	Output
1	0
0	1

 


Top View

 

3D View

 

Side View

 

1. Grow field oxide
ox.
p-type substrate
2. Etch oxide for pMOSFET
ox.
p-type substrate
3. Diffuse n-well
ox.
p-type substrate n-well
4. Etch oxide for nMOSFET
ox.
p-type substrate n-well
5. Grow gate oxide
ox.
p-type substrate n-well
6. Deposit polysilicon
ox.
p-type substrate n-well
7. Etch polysilicon and oxide
ox.
p-type substrate n-well
8. Implant sources and drains
ox.
p-type substrate n-well
9. Grow nitride
ox.
p-type substrate n-well
10. Etch nitride
ox.
p-type substrate n-well
11. Deposit metal
ox.
p-type substrate n-well
12. Etch metal
ox.
p-type substrate n-well


CMOS implementation of a buffer

• Why we need a buffer?

- Logical (virtual) representation




- Physical implementation

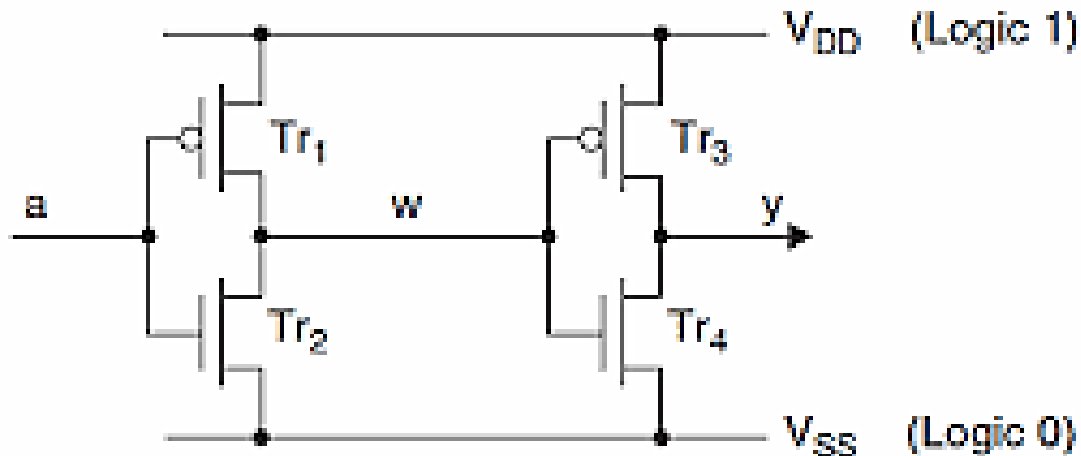


- From the logical point of view, a buffer might seem useless 逻辑上没有意义
- From the analog point of view, the buffer might have desirable characteristics such as the ability to **deliver large amounts of current** to **drive** a motor or many gates 物理上增强驱动能力
- This is an example of why we **need to consider multiple levels of abstraction** to fully understand a system; the digital abstraction hides the real purpose of a buffer.

The physical considerations


- Noise margins

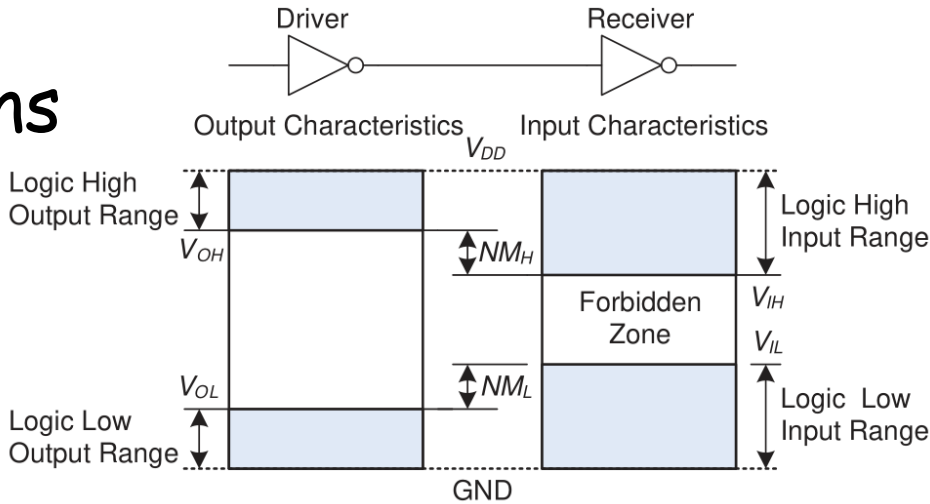


- DC transfer characteristics

 

- Physical chip

 

 - A digital clock built with 74LSxx chips



Other logic gates

异或门

XOR



$Y = A \oplus B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

与非门

NAND



$Y = \overline{AB}$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

或非门

NOR




$Y = \overline{A + B}$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

同或门

XNOR

 

$Y = \overline{A \oplus B}$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

三输入或非门

NOR3




$Y = \overline{A + B + C}$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


Digital electronics

- Combinational logic circuit

 

- Output depends on
 - Present input values
- No memory

- Sequential logic circuit

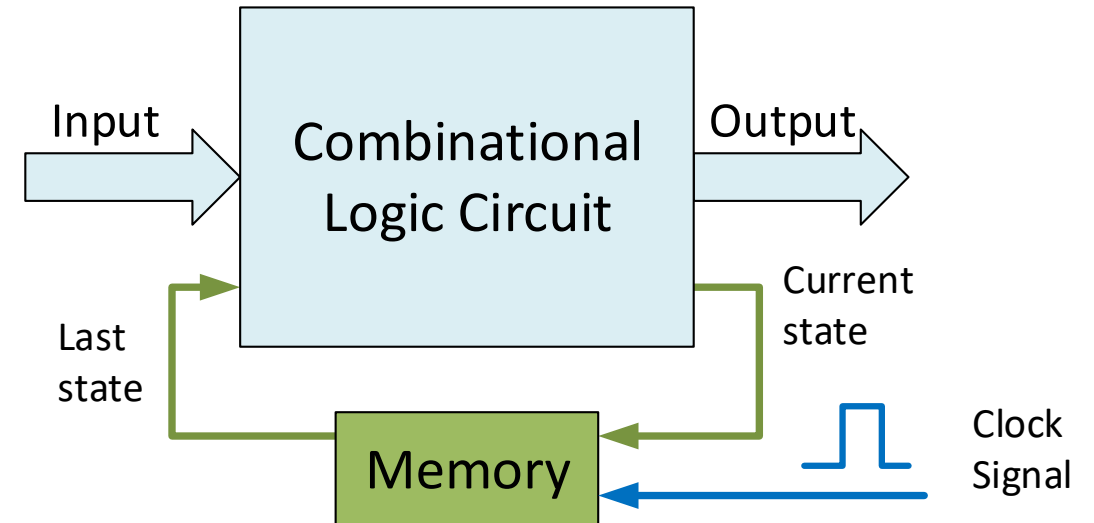


- Output depends on
 - Present inputs
 - The history of past inputs
- Have memory

Circuit implementation



- 3 input majority function
 - Truth table

S1	S2	S3	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

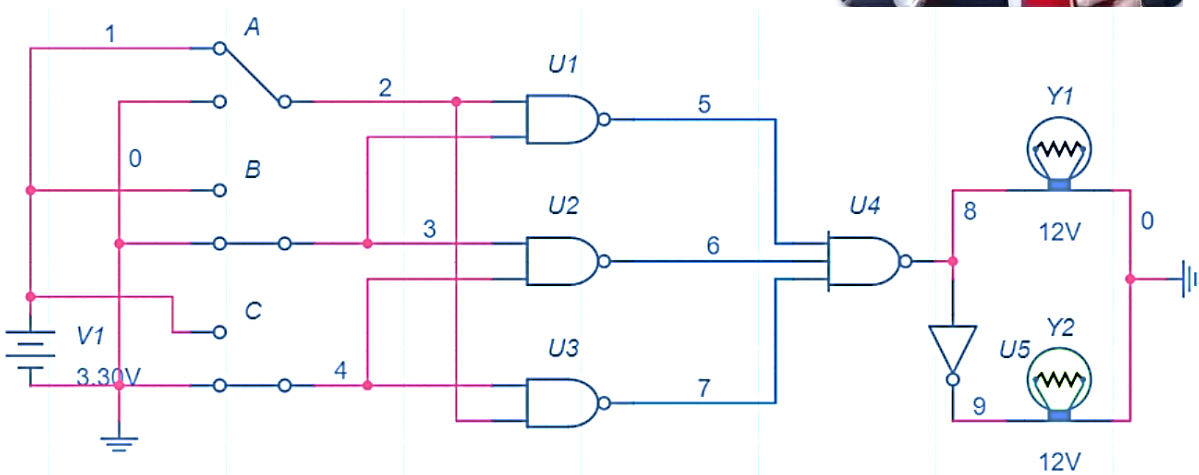

- Logic expression

$$Y = AB + BC + AC$$
$$= \overline{\overline{AB}} \overline{\overline{BC}} \overline{\overline{AC}}$$

Boolean algebra

• Axioms 公理

Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

• Theorems of two variables

Theorem		Dual		Name
T6	$B \bullet C = C \bullet B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \bullet C) + (B \bullet D) = B \bullet (C + D)$	T8'	$(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	T9'	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	T10'	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D) = B \bullet C + \overline{B} \bullet D$	T11'	$(B + C) \bullet (\overline{B} + D) \bullet (C + D) = (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots} = (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots)$	De Morgan's Theorem

• Theorems of one variable

Theorem		Dual		Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4			$\overline{\overline{B}} = B$	Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

Generalized procedures of combinational circuit design

- Improved equation minimization

Step	Equation	Justification
	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	
1	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	T3: Idempotency
2	$\overline{B} \overline{C}(\overline{A} + A) + A \overline{B}(\overline{C} + C)$	T8: Distributivity
3	$\overline{B} \overline{C}(1) + A \overline{B}(1)$	T5: Complements
4	$\overline{B} \overline{C} + A \overline{B}$	T1: Identity

- Sum of product 积(与)的和(或)
(Multiple AND terms ORed together)

- 1. $ABC + \overline{A} \overline{B} \overline{C}$
- 2. $AB + \overline{A} \overline{B} \overline{C} + \overline{C} \overline{D} + D$
- 3. $\overline{A} B + \overline{C} \overline{D} + EF + GK + H \overline{L}$

- Product of sum 和(或)的积(与)
(Multiple OR terms ANDed together)

- 1. $(A + \overline{B} + C)(A + C)$
- 2. $(A + \overline{B})(\overline{C} + D)F$
- 3. $(A + C)(B + \overline{D})(\overline{B} + C)(A + \overline{D} + \overline{E})$

Generalized procedures of combinational circuit design

- Interpret the problem and set up its **truth table**
- Write the **AND** (product) **term** for each case where output = 1
- Combine the terms in **SOP** (sum of product) form
- **Simplify** the output expression if possible
- Implement the **circuit** for the final, simplified expression

- Equation minimization example

Step	Equation	Justification
	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	
1	$\overline{B} \overline{C}(\overline{A} + A) + A \overline{B} C$	T8: Distributivity
2	$\overline{B} \overline{C}(1) + A \overline{B} C$	T5: Complements
3	$\overline{B} \overline{C} + A \overline{B} C$	T1: Identity

Karnaugh map (K-maps)



- A graphical method for simplifying Boolean equations
 - Invented in 1953 by **Maurice Karnaugh** at Bell Labs
 - Adjacent squares share all the same literals **except one**
相邻格的输入值**仅有一位**变化
 - The K-map also "**wraps around.**"
左右环接

		BC			
		00	01	11	10
A	0	1	0	1	1
	1	1	0	0	1

- Rules for finding a minimized equation:
 - Use the **fewest circles** necessary to cover all the 1's.
 - All the squares in each circle **must contain 1's**.
 - Each circle must span a **rectangular block** that is a power of 2 (i.e., 1, 2, or 4) squares in each direction.
 - Each circle should be **as large as possible**.
 - A circle may **wrap around** the edges of the K-map.
 - A 1 in a K-map **may be circled multiple times** if doing so allows fewer circles to be used.

Example: 7-segment decoder

- 7-segment display

  

(Pictures are from the Internet)


- Truth table

binary-coded decimal (BCD)


$D_{3:0}$	S_a	S_b	S_c	S_d	S_e	S_f	S_g
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	0	0	1	1
others	0	0	0	0	0	0	0

Example: 7-segment decoder

- K-map solution of S_a

 

Alternative
K-map

 

- Truth table

$D_{3:0}$	S_a	S_b	S_c	S_d	S_e	S_f	S_g
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	0	0	1	1
others	0	0	0	0	0	0	0

- Result & circuit

